

# EE242

System Verilog & FPGA's

# What's an FPGA (or CPLD)?

- Field Programmable Gate Array
- Complex Programmable Logic Device
- These are names for...
  - Programmable devices
  - Can contain lots of gates/etc.
- CPLD's often non-volatile
  - Don't need to reload them after power-up
- FPGA's may be volatile

# We'll Use: Altera MAX II


- Altera (now part of Intel) calls this a CPLD
- MAX II is a family of devices
  - Varying speed and capacity

Feature	EPM240/G/Z	EPM570/G/Z	EPM1270/G	EPM2210/G
Logic Elements (LEs)	240	570	1,270	2,210
Equivalent Macrocells	192	440	980	1,700
Maximum User I/O Pins	80	160	212	272

- Capacity
  - How much logic you can pack into the device
  - Expressed in Logic Elements
- What's a Logic Element? (next slide)
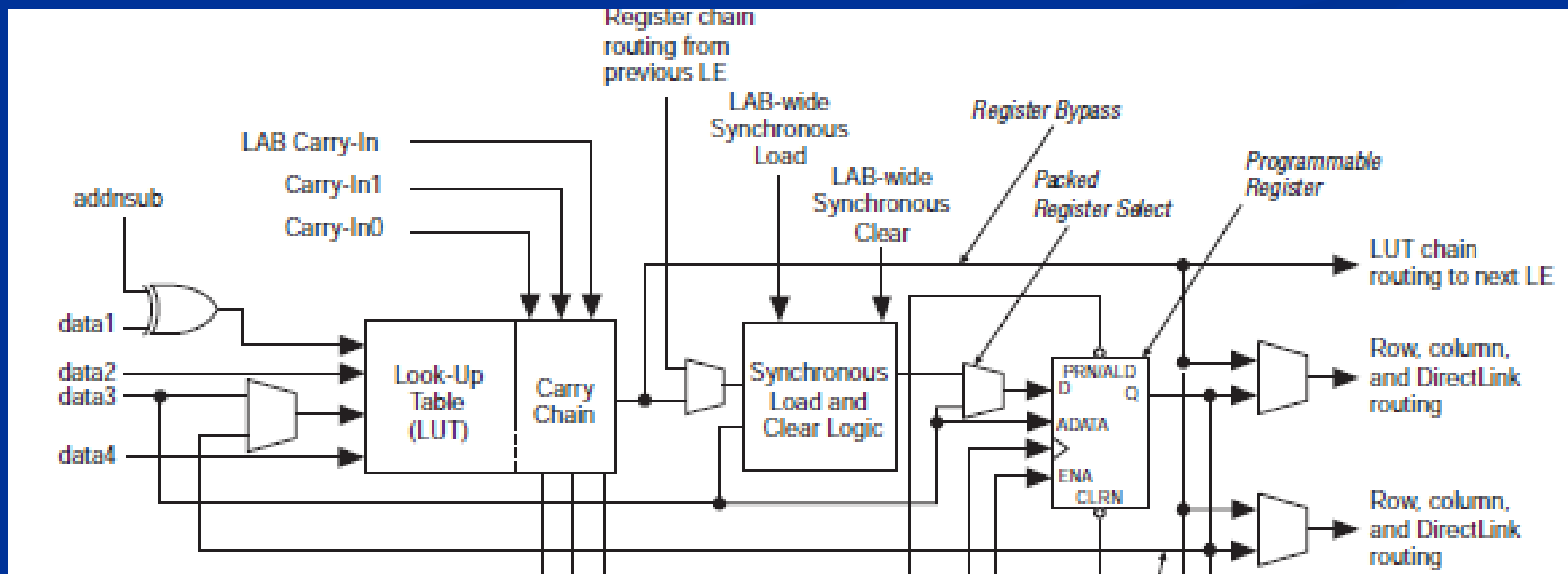
# Logic Element

- The fundamental building block in MAX II
- Contains a flip-flop
- Contains a Look Up Table (LUT)
  - Can implement any logic function of up to 4 inputs



# Working with CPLD/FPGA

- Don't worry about configuring at the LE level
  - Tools will automatically manage these
- Instead, we work at a higher level
  - Schematic capture or
  - Hardware Description Language (HDL)

# Verilog

# What's an HDL?

- Hardware Description Language
  - Use text to describe hardware
  - Alternative to schematic capture
  - Top HDL's: VHDL and Verilog
    - Some SystemC also
- VHDL
  - Looks like Ada programming language
- Verilog
  - Looks like 'C' programming language
- System C
  - Built on C++ programming language

# Verilog


- In my experience, Verilog is more common than VHDL for CPU design
- We'll use the latest variant: SystemVerilog
- IEEE standard 1800 (published 2012)
  - <http://standards.ieee.org/getieee/1800/download/1800-2012.pdf>
- This is a “big” language
  - Extends Verilog (IEEE 1364, 2005)
  - We'll only be using parts of it



# Verilog Logic Values

- Four-value logic
  - 0: logic zero
  - 1: logic one
  - Z: high-impedance (float)
  - X: contention or uninitialized

- These combine intuitively

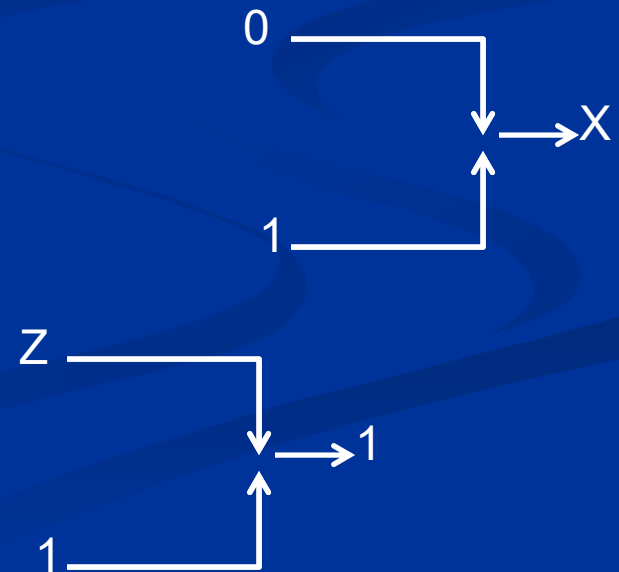

# Single-bit or Multi-bit Logic Values

- “logic” is the 4-value type
  - To “declare” is to name something, assign a type

```
        // This is a comment
logic output;           // Single-bit "output"
logic [7:0] counter;   // 8-bit "counter"
```

- Verilog code will determine what the names do
  - Flop, wire, etc.
  - We'll see this later

# Values

- Single-bit: just do it

- X, Z, 0, 1

```
output = 1;    // drive '1' onto output
triSig = Z;    // Float triSig
```

- Multi-bit: can specify length and radix

```
bus = 32'bZ;   // 32 bits of Z, 'b' = binary
value = 8'hA5; // 8b, hex
```

# Expressions

- There are *many* operators
  - We typically just use a handful of them
- The usual math expressions are available

```
x = x + 2; // add 2 to x
```

```
abc = def * 4; // def multiplied by 4
```

- Note that you can imply a lot of hardware
  - E.g., \* operator: may turn into a multiplier
  - Think about what will “come out”

# Expressions: Bitwise

## ■ $\sim$ (negation)

```
logic [7:0] x;  
x = 8'b00110101;  
x = ~x;      // x gets 11001010
```

## ■ $\&$ , $|$ , $\wedge$ (and, or, exclusive-or)

```
logic [7:0] x, y, z;  
x = 8'b11000011;  
y = 8'b00000010;  
z = x & y;      // z gets 00000010  
z = x | y;      // z gets 11000011  
z = x ^ y;      // z gets 11000001
```

# Expressions: Relational

```
logic rel;
```

```
rel = A == B;    // rel is '1' if A equals B
```

```
rel = A != B;    // rel is '1' if A not equal B
```

```
...
```

# Combinatorial Logic Modules

# Combinatorial Logic

- Also known as
  - Random logic
  - Combinational logic
- AND, OR, etc...
  - Equations, or expressions
- Verilog has certain places where you can put these



# always\_comb

- Used to contain logic that is *only* combinatorial
  - Not flip-flops or latches
- Example (from an EE345 CPU)

```
always_comb begin
    valid = memAccess.op.size != szNone; // non-0 # of bytes to access
    memReq.memRd = valid & memAccess.op.isLoad;
    memReq.memWr = valid & ~ memAccess.op.isLoad;
    // ...
end
```

Combinatorial equations

Note: “blocking” assignment uses “=”. Effect is for assignments to happen in order.

# Modules


- A “module” is like an IC for Verilog
  - Collection of logic
  - Defined inputs/outputs (ports)
  - May be instantiated multiple times

```
module Inverter(  
    input logic in,  
    output logic out  
);  
    always_comb out = ~in;  
endmodule
```

Begin/end of module

ports

body

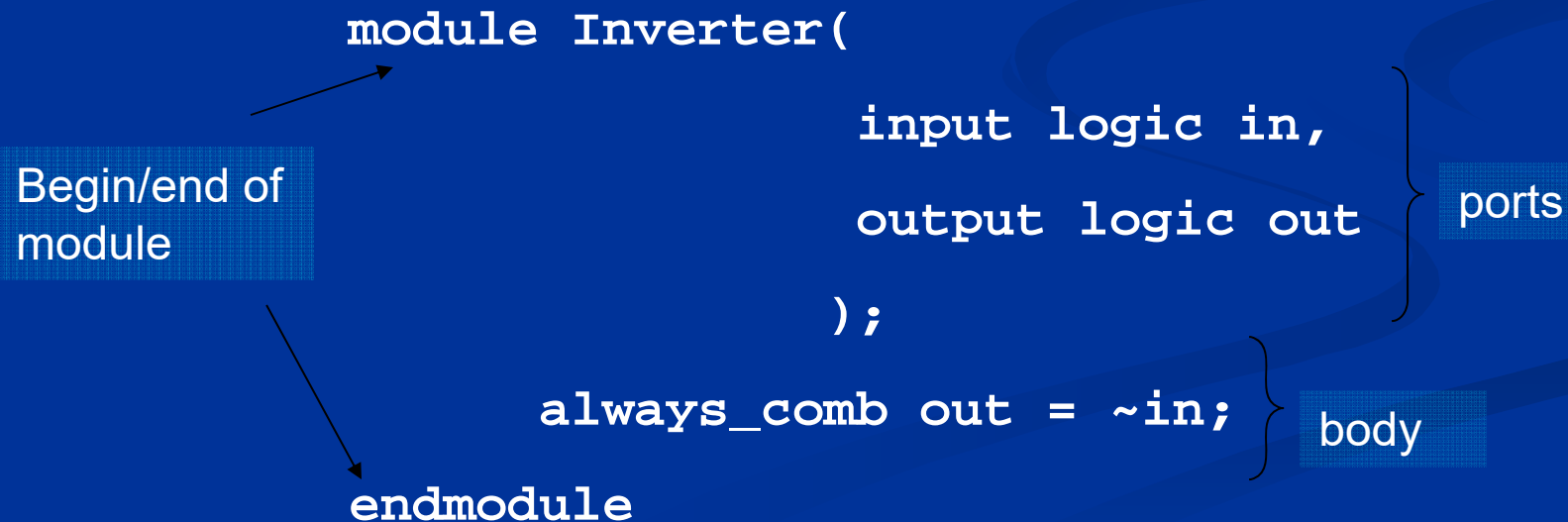

# Using Modules

- Create an instance, connect ports

```
logic sigInput, sigOutput;
```

```
Inverter inv1(  
    sigInput, // in  
    sigOutput // out  
);
```



# Modules and MAX II

- When creating a design for MAX II...
  - Make it a module
- The ports names are the pins on MAX II

```
module top(  
    input logic in,  
    output logic out  
);  
    always_comb out = ~in;  
endmodule
```

Convention: main module named "top"

"in" and "out" will be the pins on your MAX II design

# Sequential Logic

# Always\_ff

- Controls code that results in flops
- You supply “sensitivity” list
  - Signals that can change the flop’s state
  - Usually just a clock

```
always_ff @(posedge clk)  
    // put logic here
```


- Flops trigger on clock edges
  - Can specify *posedge* or *negedge*
  - We normally uses *posedge*

# Example: D flop

- Output Q gets value of D on positive edge
- Maintains value until next positive edge

```
always_ff @(posedge clk)
```

```
q <= d;
```

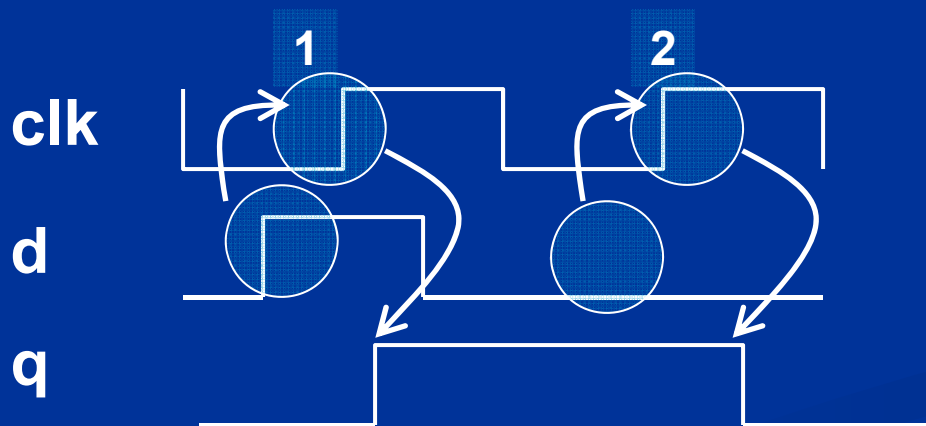

At edge 1

- q follows d to 1

At edge 2

- q follows d to 0

# What's up with $\leq$ ?

- “ $\leq$ ” is another assignment operator
  - “non blocking assign”
- “ $=$ ”: assignments happen in linear order
- “ $\leq$ ”: happen in random order
- Use “ $=$ ” for combinational logic
  - Because you're building up layers of logic
  - Gate A feeds gate B: evaluate “A =” before “B = A...”
- Use “ $\leq$ ” for sequential logic
  - Because everything happens next clock



# Example: Synchronous Reset

- Synchronous reset is preferred
  - Avoid metastability/race issues
  - Map into more PLD/FPGA devices

```
always_ff @(posedge clk)
    if(rst)
        q <= 0;
    else
        q <= d;
```


# Example: Binary Counter

- Looks like an adder
- Tools will optimize into counter

```
always_ff @(posedge clk)
    count <= count + 1;
```
 
# Example: Shift Register

- Shift register moves data one step on each clock




```
logic [3:0] sreg;
always_ff @(posedge clk)begin
    sreg[0] <= in;
    sreg[1] <= sreg[0];
    sreg[2] <= sreg[1];
    sreg[3] <= sreg[2];
end
```

```
logic [3:0] sreg;
always_ff @(posedge clk)
begin
    sreg[0] <= in;
    sreg[3:1] <= sreg[2:0];
end
```
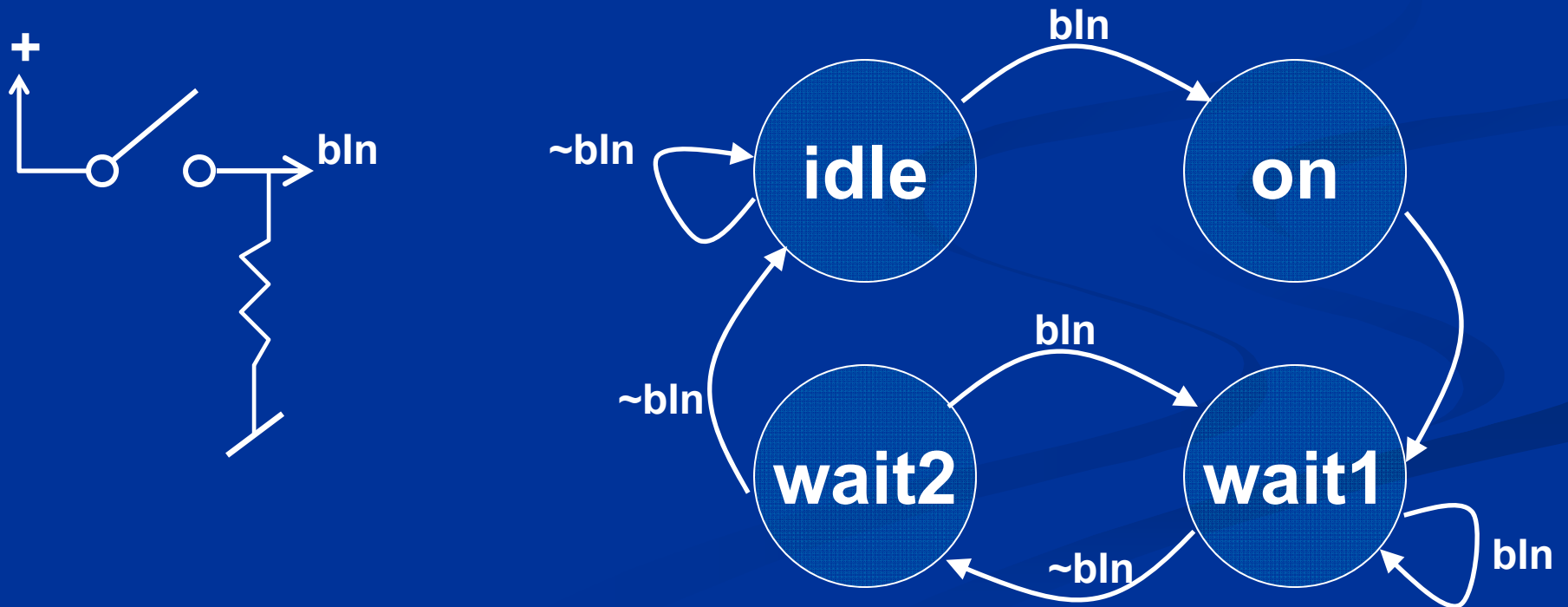
# Example: state machine

- Debounce a switch
  - switch pressed:  $bIn$  is 1
  - “Bounce” if  $bIn$  has short pulse after switch released



# Example: State Machine

```
module Debounce (
    input logic clk,           // 10-20 Hz for debounce
    input logic bIn,          // 1 = "button active"
    output logic pressed      // 1 = button-press
);
    enum          {idle, on, wait1, wait2 } state;

    always_ff @(posedge clk)
        case(state)
            idle: state <= bIn ? on : idle;
            on:   state <= wait1;
            wait1: state <= bIn ? wait1 : wait2;
            wait2: state <= bIn ? wait1 : idle;
        endcase

    assign pressed = (state == on);
endmodule // Debounce
```