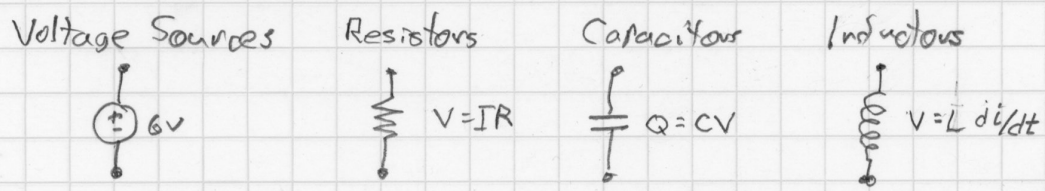


EE 251 Electronics I Introduction, Diodes

So, what's the difference between "electric" and "electronic"?

In "electric" circuits we have our usual well known components:



And many others: Motors, Transformers, Current Sources

These components are connected to nodes with wiring to build a circuit which performs some function, such as propelling a vehicle, lighting a room at house, etc.

These circuits are governed by fundamentals from Physics - Kirchoff's Current law, Kirchoff's Voltage law, Thevenin & Norton's Theorems, many others.


(Usually, or at least often, we have "linear" circuits in which the principle of Superposition holds and we can "solve" circuits with Linear System Theory.)

An "electronic" circuit, originally defined, was an electric circuit that had, in addition to the usual electric components, also "electronic" components.

So, what is an "electronic" component, and what's different?

Original electronic components had current flowing entirely by the movement of electrons in gas/vacuum - where there was no obvious physical connection

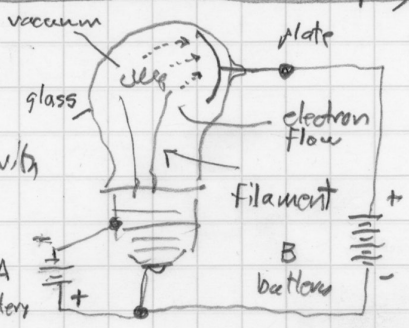The original "diode":
light bulb with extra element "plate"





Notice: These are "free electrons" not bound to atoms. The world changed!

Observation: If the "B Battery" is positive toward the plate, and negative toward the filament, current flows!
 If the "B Battery" is negative toward the plate and positive toward the filament - no current!

That's because: Hot filament throws off electrons, but the plate only attracts them if it is "more positive" than the filament.

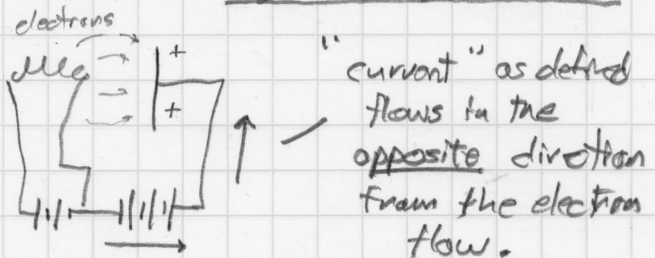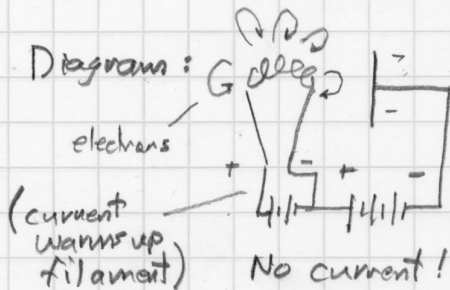
So, electrons must be negative charge carriers!



The electron device is called a "diode": It conducts electricity in only one direction.


In today's world, diodes are built from semiconductors.

Silicon:

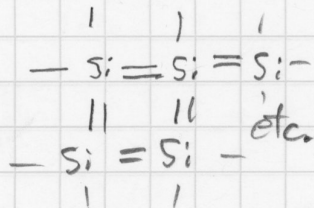


Silicon (and Germanium, various others) form bonds with adjacent atoms in a crystalline structure. For Si, Ge, 4 bonds (Both are in column IV of periodic table)

Silicon with Arsenic impurity:

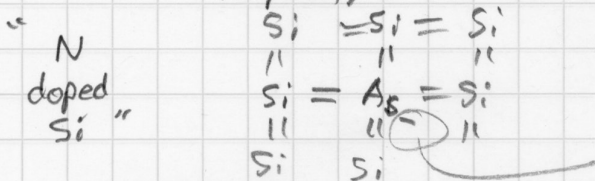

It's possible for electrons to get knocked loose, but not easy, unless there are impurities - say Al (III) or As (V)

Silicon with Al:

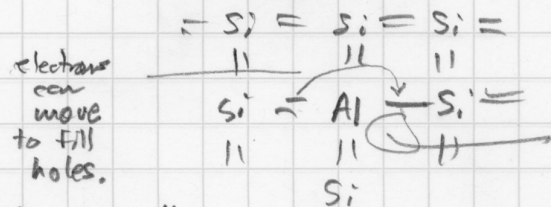


P doped Si"


With a lone As in the Si matrix, there's a loose electron that's not tightly bound. In an electric field, it will move - conduct

With Al in Si matrix, there is a "hole" in the matrix that wants to be filled. In an electric field, the hole moves - conducts.

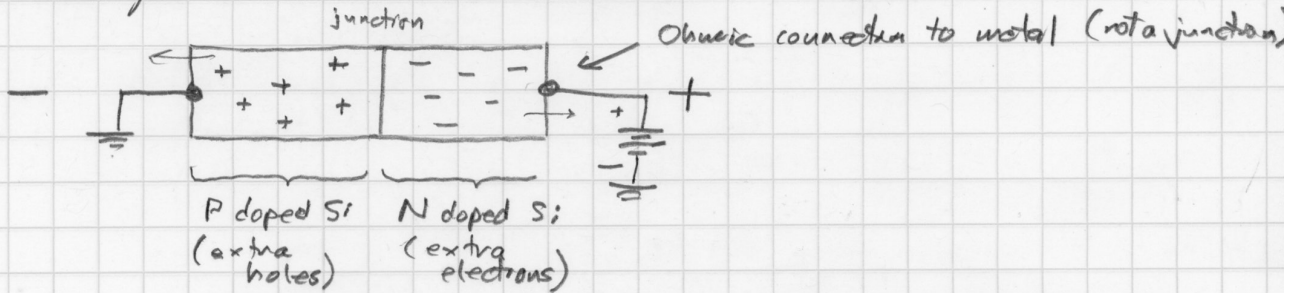With two pieces of "doped" silicon brought together at a "junction" we get a semiconductor diode =




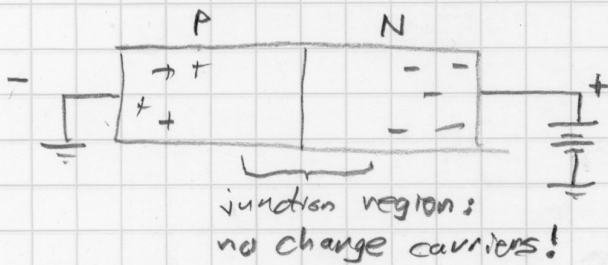If we put a positive field from P to N - No current flows!
The holes head away from junction, and electrons too



With no charge carriers in the junction region, current can't flow!
(Bulk material away from junction has to be electrically neutral, so still some there.)

(Note: Looks like small capacitor)

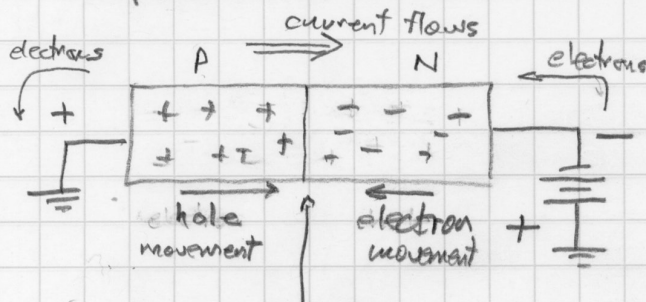


At junction, the electrons fall into the holes!
(Can emit photons in some cases, eg. LEDs)

As holes + electrons mutually annihilate each other at the junction, additional electrons get injected into the N material and pulled out of the P materials & continuously keep charge carriers moving. Current flows!

We abstract all this into a symbol for the part and a "model" for its behavior:

"anode"

"cathode"


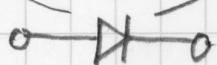


physical device:



↳ stripe at cathode end

Simplest model:

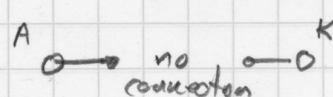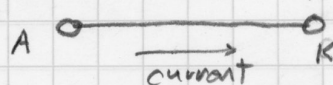


(symbol "K" often used for cathode)

"ON" if current flows from anode to cathode

"OFF" if $V_K > V_A$
no current
"open"

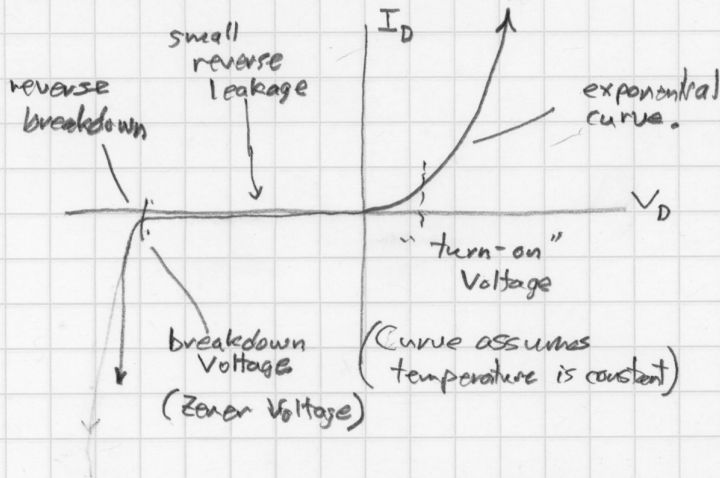Actual diode devices behavior can be graphed with an I vs V curve:



Real semiconductor diodes have approximately exponential forward behavior - Current increases very rapidly beyond some nominal "turn on" voltage.

At some reverse Voltage the diode "breaks down" and starts conducting in the reverse direction

In most circuits, reverse breakdown is undesirable. It will usually cause high dissipation which the diode is not designed to handle.

Because Electrical Engineering is an analytic discipline, we use mathematical models to represent diodes in circuits, so that we can use circuit principles to solve for circuit behavior, or to put into circuit simulations.

"Diode equation" (book Eq. 1.18 p.28.)


$$i_D = I_s \left[e^{\frac{v_D}{nV_T}} - 1 \right]$$

Annotations: v_D is a variable; I_s and nV_T are constants.


Note: Does NOT model the reverse breakdown behavior, but IS good for both positive and negative values of v_D .

At negative v_D approaches 0
 At zero $v_D = 1$
 At positive v_D gets big exponentially

Reverse leakage current

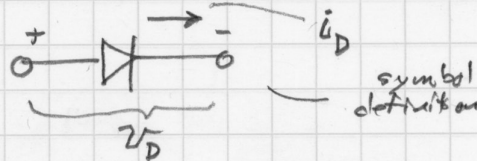

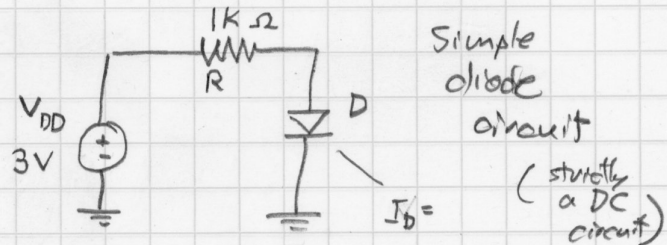Note also: v_D - lower case represents instantaneous to total Voltage (AC+DC)



Simple diode circuit (strictly a DC circuit)

loop equation: $V_{DD} = v_R + v_D \Rightarrow 3V = 1k\Omega \cdot i_D + nV_T \cdot \ln\left(\frac{i_D}{I_s} + 1\right)$


one equation, solve for i_D ← (can you solve this?)

Using the diode equation to solve a circuit:

$$3V = 1K\Omega \cdot i_D + n \cdot V_T \cdot \ln\left(\frac{i_D}{I_S} + 1\right)$$

How? :)

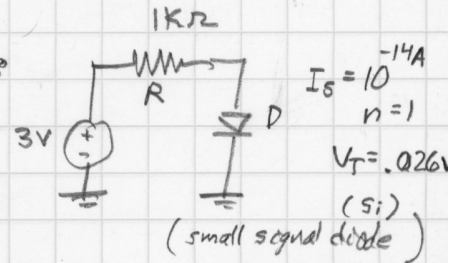I'm going to use "successive approximation"



Step

1. I'll assume that, since Si, $V_D = .7V$, solve for i_D :

$$3V = 1K\Omega \cdot i_D + .7V \Rightarrow i_D = 2.3mA \quad \leftarrow \text{equal?}$$

2. Now calculate V_D for $i_D = 2.3mA$: $i_D = 10^{-14} A \cdot e^{.7V / .026V} - 1 = 1.8mA$
 pretty close, but actual V_D must be larger.

3. I'll assume actual V_D is higher by $.01V$: $.71V$ rather than $.7V$

$$3V = 1K\Omega \cdot i_D + .71V \Rightarrow i_D = 2.29mA \quad \leftarrow \text{equal?}$$


4. Now calculate V_D for $i_D = 2.29mA$: $i_D = 10^{-14} A \cdot e^{.71V / .026V} - 1 = 2.66mA$
 closer, but went too far. That

$.01V$ change caused a $.86mA$ change in i_D ! (only needed $+.5mA$)

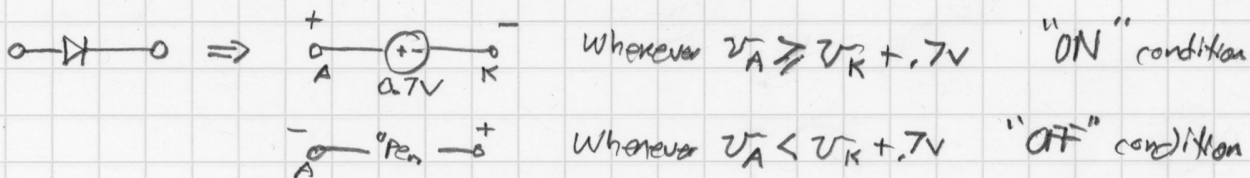5. I'll take just $(.5 / .86) \times .01V$ so now assume $V_D = .706V$:

$$i_D = 10^{-14} A \cdot e^{.706V / .026V} - 1 = 2.28mA \quad \text{close enough!}$$

In fact, our original guess of $.7V$ for V_D wasn't bad at all! So, this suggests a simpler model for this diode:




This will be pretty close as long as i_D is in the range of about $1\mu A$ up to several mA .

A refinement of that model would represent the AC resistance of the diode - how much is $\Delta V / \Delta i_D$

$$\text{From calculations above, } .01V / .86mA = 11.6\Omega$$

So

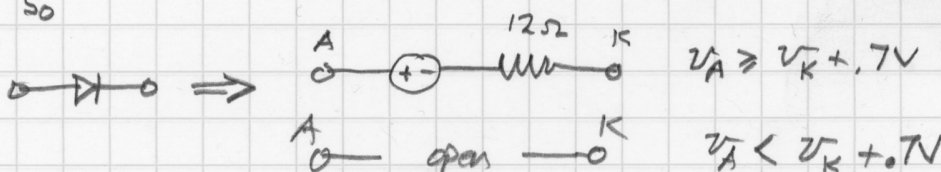


So, now that we have diode devices, what can we do with them?

#1 Power application - Change AC to DC to charge batteries:

AC is used by modern electric utilities so that they can use transformers to allow high voltages for transmission, thus reducing conductor sizes needed, for greater efficiency. But, that's fine for incandescent light bulbs, but need DC for battery charging or to run DC motors, DC for electronics!



Battery Charger Circuit:

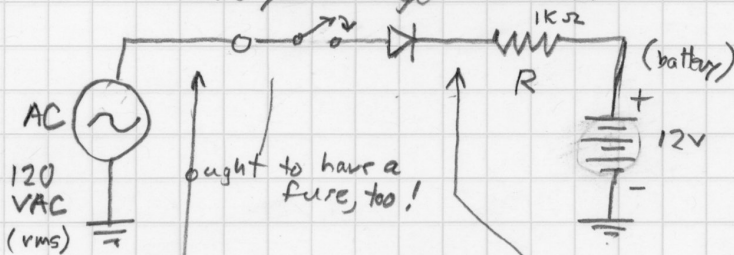Assume $V_{D_{on}} = 0.7V$ (silicon)
 $R = 1K\Omega$



$$\text{peak } I_D = \frac{170V - 0.7V - 12V}{1K\Omega} = 157.3 \text{ mA}$$

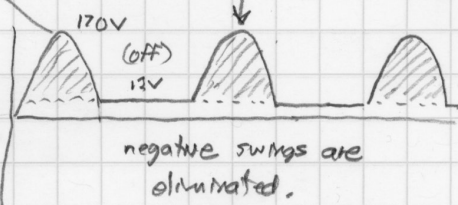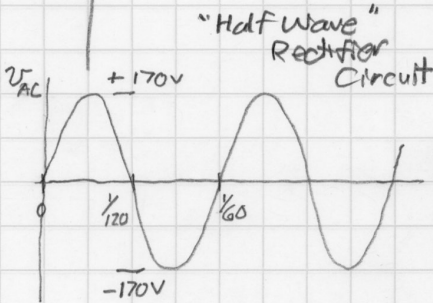What is average charging current? Integrate areas shown and divide by T to find it.




(Approx.)

$$\frac{157.3 \text{ mA}}{2\sqrt{2}} \approx 55 \text{ mA}$$

This is called a "Rectifier" circuit

(Diodes designed for this are called "Rectifier Diodes" or just "Rectifiers")

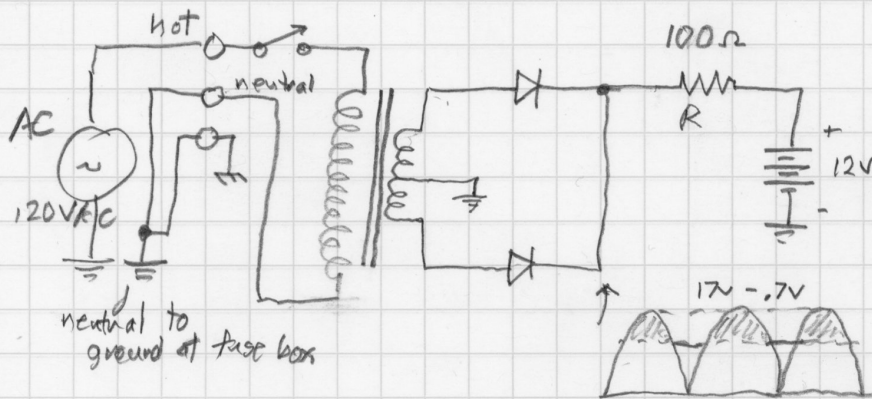
A Better circuit (more efficient) uses a transformer (to reduce lost power in the resistor, and to allow full wave rectifier




The transformer converts the negative swing to positive with lower half of secondary - doubles the current to the "load"

(Trickier to integrate now)

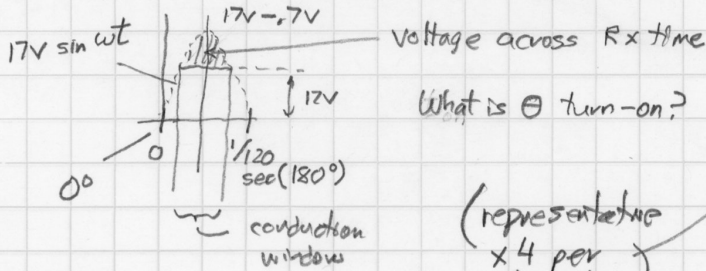Full wave rectifier battery charger - We'd like to find average current





(representative x 4 per AC cycle.)

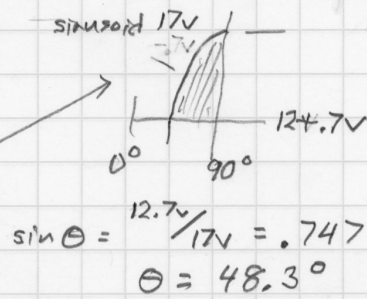

Batteries really don't care about variations in current - it's the total charge accumulated that matters. (Mostly - don't go to extremes though.)

BUT We'd like, for many applications, to have smoother DC


With 3Ø systems, we can get that:

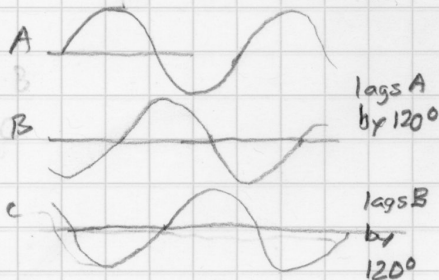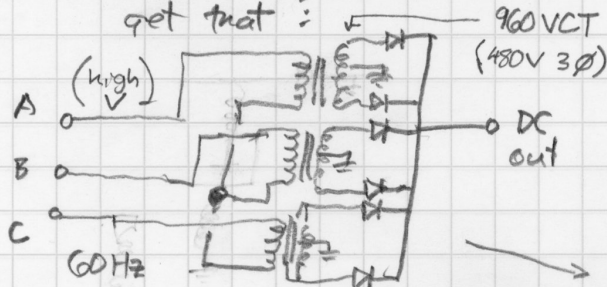

$$\begin{aligned} \bar{V}_R &= \int_{48^\circ}^{90^\circ} (\sin \theta \cdot 17V + 12.7V) d\theta \times \frac{1}{90^\circ} \\ &= \frac{-\cos \theta \cdot 17V}{90^\circ} \Big|_{48^\circ}^{90^\circ} - \frac{12.7V \theta}{90^\circ} \Big|_{48^\circ}^{90^\circ} \\ &= \frac{0 + .669 \cdot 17V}{90^\circ} - 12.7V \left(\frac{42^\circ}{90^\circ} \right) \\ &= \left(\frac{38.3^\circ}{90^\circ} \right) \cdot 17V - \\ &= (.426 \times 17V) - 5.927V \\ &= 7.24 \end{aligned}$$


= 1.315 V average across 100Ω

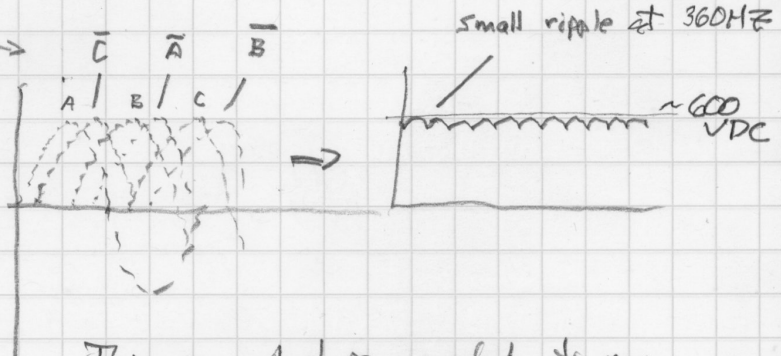so $I_{AVERAGE} = 1.315V / 100\Omega = 13.15mA$




This is what is needed to run an electric trolley car. You also see this in other power applications where variable speed drive is wanted

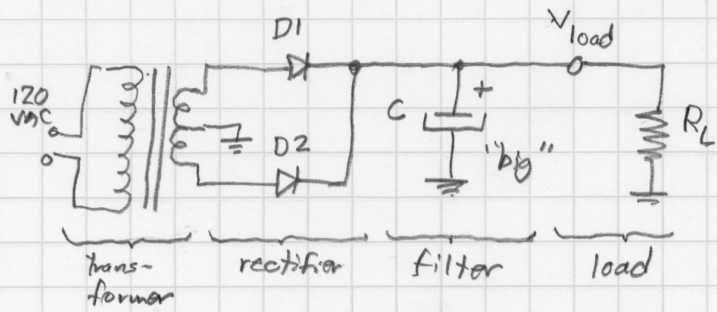Getting smooth DC from a Rectifier Circuit - Capacitor Filter!



- Assuming:
- 1) Lossless transformer (real ones have resistance)
 - 2) $V_{D_{on}} = 0.7V$
 - 3) C is "big" (shunts out AC to ground)

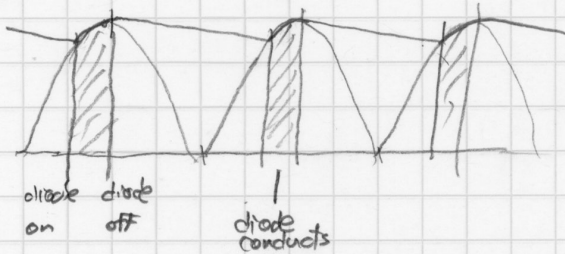Then $V_{Load} = V_{peak}(trans \times \frac{1}{2}) - 0.7V$



When diode is on, it supplies current to the load AND recharges the capacitor to its maximum voltage

When diode is off, the capacitor supplies all of the current to the load. (Sort of like a battery)

Theoretically, a battery could do this job, but batteries wear out from cycling up and down. This circuit cycles at 120Hz! Batteries aren't going to like that!

So, with 120VAC, transformer is 24VCT (center tapped) so each side gives 12VAC (17Vpeak). After the diode, that is reduced to 16.3V peak (Assuming $V_{D_{on}} = 0.7V$)

Suppose $R_L = 1000\Omega$, $C = 1000\mu F$. How much "ripple" do we get?


Let's make this easy. C values are typically only accurate to +/- 20%. So, we will assume the C discharge time goes the full 1/120 sec between charging spikes, and the output voltage is 16VDC (we know it can't be more than 16.3V)

$$I_C = I_L = \frac{16V}{1000\Omega} = 16mA \quad Q = CV \text{ so } I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

Because ΔT is short compared to exponential time constant $RC = 1 \text{ second}$,

$$I = C \frac{\Delta V}{\Delta T} \quad \text{where } \Delta T = 1/120 \text{ sec}$$

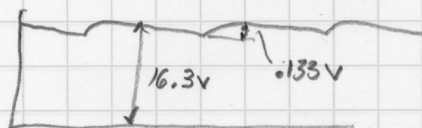
$$\Delta V = \frac{1}{120 \text{ sec}} \frac{16mA}{1000\mu F} = 0.133V$$



So voltage will "droop" about 0.13V between peaks.

Pretty good (about 1%)

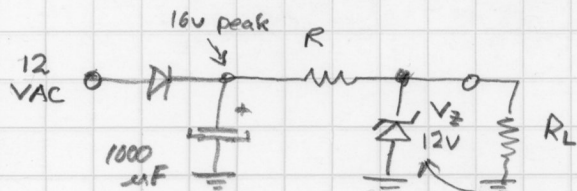Sometimes we want very precisely controlled DC Voltages — achieved with a "Regulator" circuit. There are 2 basic kinds — "Series" regulators and "Shunt" regulators:



Basic Shunt Regulator

(We won't cover series regulators because they need transistors. Series regulators typically require a shunt regulator internally.)

notice the modified symbol ~~to~~

This circuit uses the "breakdown" region of a diode.

A "Zener diode" is a diode designed to work in this manner, and is sold to operate and give a fairly precise Voltage, typically about 5V or higher, and also large enough to handle the good bit of heat from the power dissipated

V_Z is the reverse breakdown "Zener" voltage of the diode

So, match the diode to the desired output Voltage.

Choose the regulator resistance R so that at the minimum Voltage from the filter, you get enough current to supply the maximum load (minimum R_L).

We'll assume minimum $R_L = 500\Omega$, so at 12V, 24mA with 24mA, that 16V peak will droop to about 15.8V

$$\text{So } (15.8\text{V} - 12\text{V}) / 24\text{mA} = 158\Omega \quad (\text{we'll use } 150\Omega)$$

(How much power does it have to handle? $\approx 100\text{ mW}$ or so.)

The rectifier will deliver about 25mA to the regulator.

Any at that which doesn't go to the (variable) load gets dumped into the Zener diode — as much as






$$12\text{V} \cdot 25\text{mA} = 300\text{ mW} \quad (\text{Most Zeners are good for } \approx 1/2\text{ W})$$

(If load is open, that's all of the power supplied.)


(A better model for a Zener includes a small bit of resistance, too.)

Other diode applications:


AM Radio demodulator:

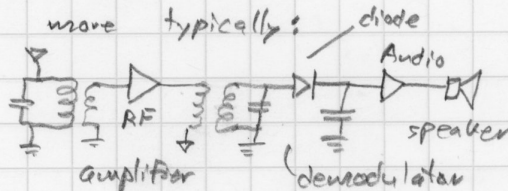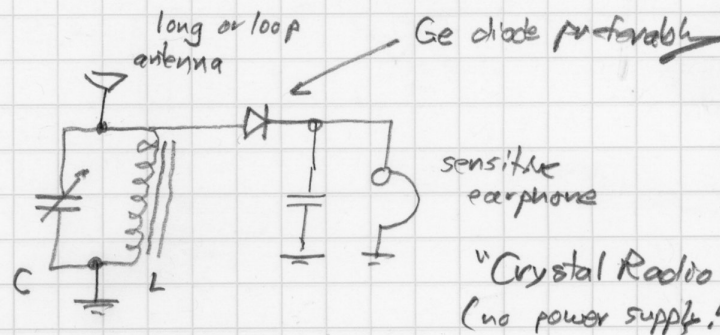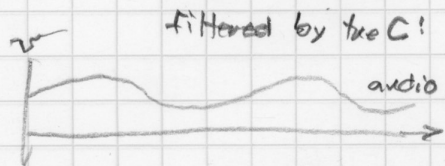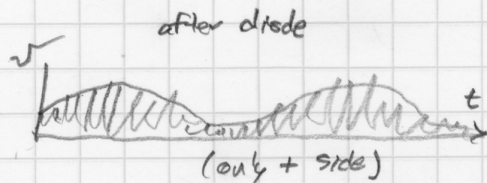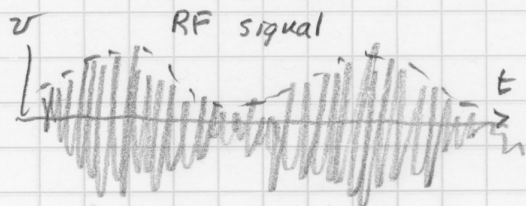


For FM

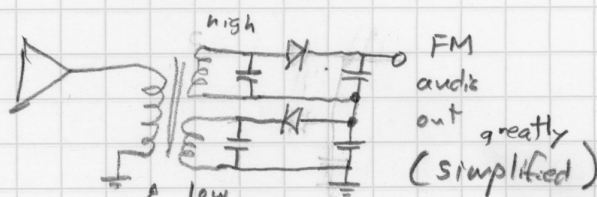

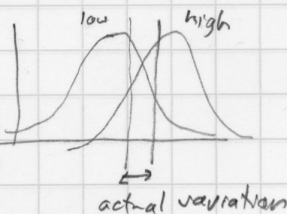
Two AM detectors but resonant at different frequencies. Take the difference in amplitude as the audio signal out.




Voltage Double Rectifiers:

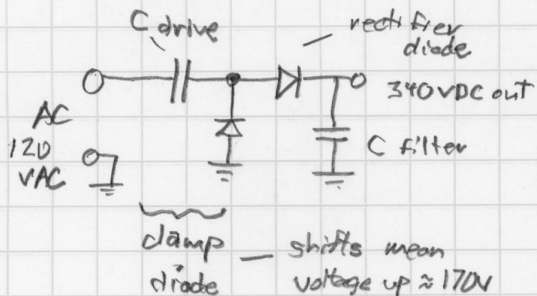



(This was used in 1960's TV sets)

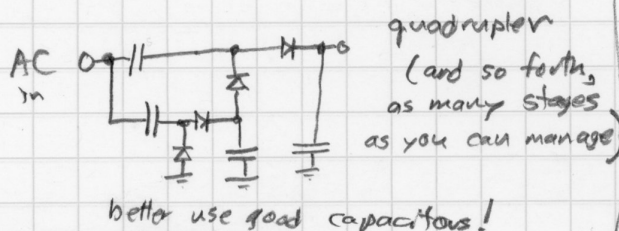

LED's:

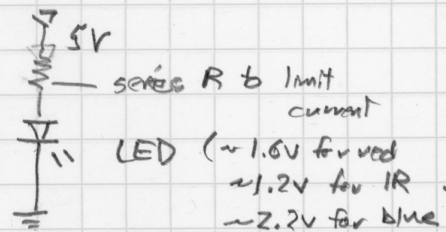

Silicon Controlled Rectifiers:

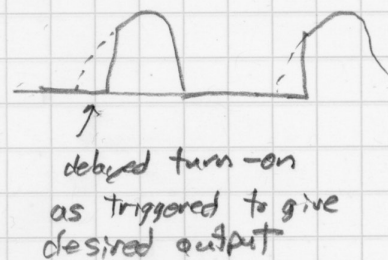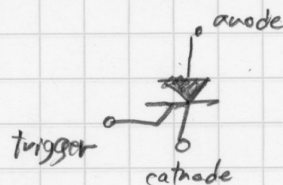

Opto isolators:

