

EE283 Lab 4 Superposition And Thevenin, Norton Analysis

Objective: The object of this exercise is to

- Verify the superposition principle.
- Use Thevenin and Norton equivalent circuits to simplify circuits.

Equipment Required:

- Digital Multimeter (DMM Keysight 34461A)
- Resistor Decade Box
- Resistor Color Codes (see appendix A)
- Power Supply (Keithley 2231A-30-3)
- Breadboard

Superposition Theory:

The total current in any part of a linear circuit equals the algebraic sum of the currents produced by each source separately. To evaluate the separate currents to be combined, replace all other voltage sources by short circuits and all other current sources by open circuits.

Procedure:


- Use the DMM to measure the voltage at node A with both voltage sources turned on. Then measure the voltage at node A with V_{S1} removed and replaced with a short circuit. Then measure the voltage at node A with V_{S2} removed and replaced with a short circuit and V_{S1} reinstalled and set to the original voltage.

Step number

1. Using the resistors supplied, measure the resistance values using the DMM and record the values and tolerances in the table below and in your report. Then construct the circuit below on your breadboard.

Reference Designation	Nominal Resistance value – Ohms	Actual Resistance Value – Ohms	Resistor Tolerance %
R ₁	680		
R ₂	1K		
R ₃	470		

Table 1

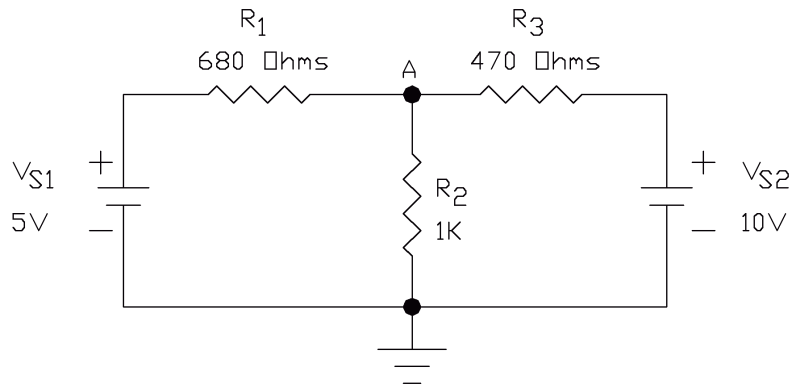

Step 1 setup figure

- Set the voltage of V_{S1} to $+5 V_{DC}$ and set the voltage of V_{S2} to $+10 V_{DC}$. Using the DMM set to measure V_{DC} measure the voltage at node A. Record this voltage in the table below. Repeat this measurement with $V_{S1} = +5 V_{DC}$, $V_{S2} = 0 V_{DC}$ (i.e. replace V_{S2} with a short circuit) and again with $V_{S1} = 0 V_{DC}$ (i.e. replace V_{S1} with a short circuit), $V_{S2} = +10 V_{DC}$. Record these values in your report.


Column 1	Column 2	Column 3
$V_{S1}=5 V_{DC}$ $V_{S2}=10 V_{DC}$	$V_{S1}=5 V_{DC}$ $V_{S2}=0 V_{DC}$	$V_{S1}=0 V_{DC}$ $V_{S2}=10 V_{DC}$

Table 2


Add the voltages in columns 2 and 3. Does the sum of these voltages equal the voltage in column 1? Show this summation in your report.

Thevenin and Norton Equivalent Circuit Theory:

A Thevenin circuit is a voltage source connected in series with a resistor. This Thevenin circuit can be converted to a Norton equivalent circuit which is a current source in parallel with a resistor. The current source will have the value of the Thevenin voltage source divided by the Thevenin resistance. The Norton equivalent resistance will have the same value as the Thevenin resistance. This is shown in the figure below. An external linear component (i.e. a resistor, inductor or capacitor) connected between terminals A and B will have the same voltage and current no matter which circuit it is connected to. The Norton circuit is equivalent to the Thevenin circuit.

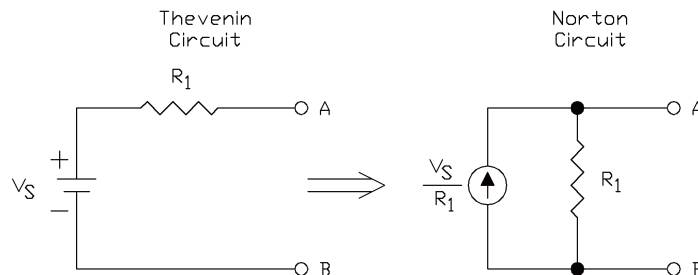

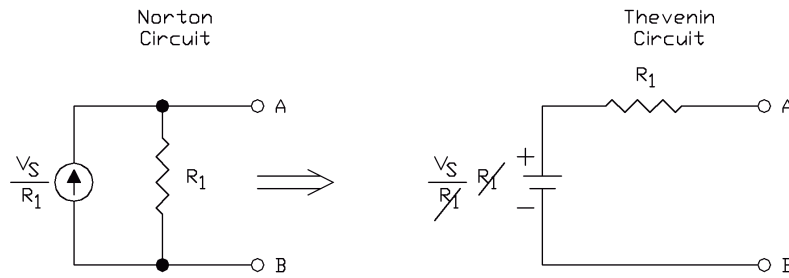In a similar manner a Norton circuit can be converted into a Thevenin equivalent circuit as shown in the figure below.



The Thevenin equivalent voltage source will have the value of the Norton current source multiplied by the Norton resistance. The Thevenin equivalent resistance will have the same value as the Norton resistance. The Thevenin circuit is equivalent to the Norton circuit.


Procedure:

- Using the resistors supplied, measure the resistance values using the DMM and record the values and tolerances in the table below and in your report. Then construct the circuit below on your breadboard.

Reference Designation	Nominal Resistance value – Ohms	Actual Resistance Value – Ohms	Resistor Tolerance %
R ₁	2.7K		
R ₂	2.2K		
R ₃	470		
R _L	1K		

Table 3

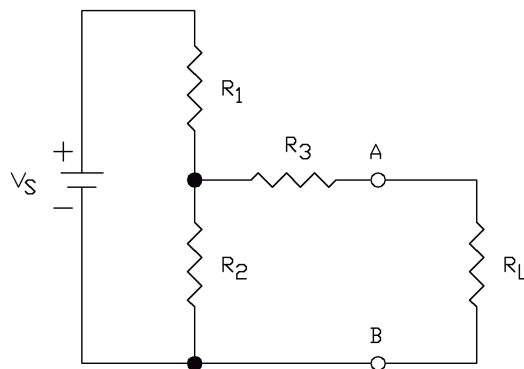- Construct the circuit shown below on your breadboard. Set the power supply voltage, V_S to +10 V_{DC}.




Step 4 setup figure

5. With the DMM set to measure V_{DC} measure the voltage from A to B (V_{A-B}) for the following three conditions and record these voltages in the table below and in your report.
- With R_L removed
 - With R_L shorted
 - With R_L installed

	R_L removed	R_L shorted	R_L installed
V_{A-B}			

Table 4

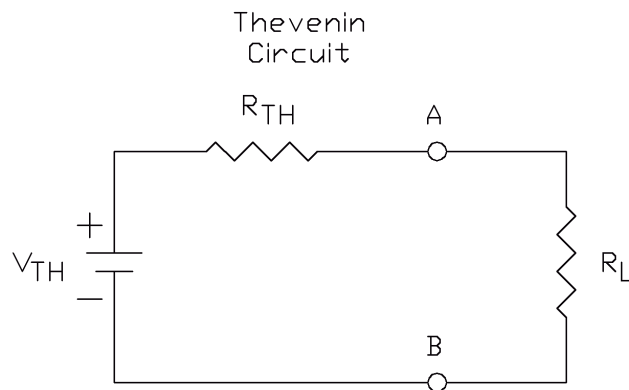6. Using the measured values of V_S , R_1 , R_2 and R_3 shown in Table 3 determine the values for Thevenin equivalent circuit shown below. Show your calculations in your report. Mark these values on the circuit below and in your report.



Thevenin equivalent circuit

7. Construct the Thevenin circuit using a resistance decade box set for the value of the Thevenin resistance, R_{TH} . Set the power supply voltage to the Thevenin voltage, V_{TH} .
8. With the DMM set to measure V_{DC} measure the voltage in the Thevenin circuit from A to B (V_{A-B}) for the following three conditions and record these voltages in the table below and in your report.
- With R_L removed
 - With R_L shorted
 - With R_L installed


	R_L removed	R_L shorted	R_L installed
V_{A-B}			

Table 5

9. In your report compare the voltages in tables 4 and 5. Do they agree? If not why not?

Remember that your report must be legible. If I can't read it you won't get credit for it!

Appendix A

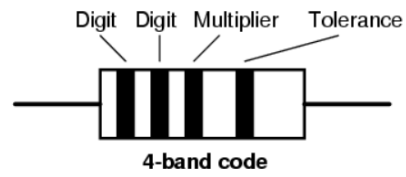

Color	Digit	Multiplier	Tolerance (%)
Black	0	10^0 (1)	
Brown	1	10^1	1
Red	2	10^2	2
Orange	3	10^3	
Yellow	4	10^4	
Green	5	10^5	0.5
Blue	6	10^6	0.25
Violet	7	10^7	0.1
Grey	8	10^8	
White	9	10^9	
Gold		10^{-1}	5
Silver		10^{-2}	10
(none)			20

EE283 Laboratory Exercise 4 Form Report

Name: _____ Section: _____ Station: _____ Date: _____

Reference Designation	Nominal Resistance value – Ohms	Actual Resistance Value – Ohms	Resistor Tolerance %
R ₁	680		
R ₂	1K		
R ₃	470		

Resistor tolerances and measured resistance from step 1
Table 1

Step 1 setup figure here

Column 1	Column 2	Column 3
V _{S1} =5 V _{DC} V _{S2} =10 V _{DC}	V _{S1} =5 V _{DC} V _{S2} =0 V _{DC}	V _{S1} =0 V _{DC} V _{S2} =10 V _{DC}

Node A voltage readings from step 2
Table 2

Add the voltages in columns 2 and 3. Does the sum of these voltages equal the voltage in column 1? Show work here.

Reference Designation	Nominal Resistance value – Ohms	Actual Resistance Value – Ohms	Resistor Tolerance %
R ₁	2.7K		
R ₂	2.2K		
R ₃	470		
R _L	1K		

Resistor tolerances and measured resistance from step 3
Table 3

Step 4 setup figure here

	R_L removed	R_L shorted	R_L installed
V_{A-B}			

V_{A-B} voltages from step 5
Table 4

Show calculations for Thevenin equivalent circuit components V_{TH} and R_{TH} here.

Show Thevenin equivalent circuit here

	R_L removed	R_L shorted	R_L installed
V_{A-B}			

V_{A-B} voltages from step 8
Table 5

Compare the voltages in tables 4 and 5 here. Do they agree? Yes/No. If No why not?